

The diagram illustrates a simple series electrical circuit. It consists of a battery (cell), a light bulb, and a switch connected in a single loop by wires. Crocodile clips are used to connect the wires to the components. The circuit is labeled 'Complete Circuit'. The components are labeled: wire, cell, battery, connection, crocodile clip, bulb, switch, and motor.

Simple Series Electrical Circuit	
complete circuit	A complete loop with electricity flowing the way it is supposed to flow.
cell	A single source of stored power.
battery	One or more cells together form a battery that gives power.
connection	Joining 2 or more components together.
crocodile clip	Sprung metal clip with teeth used to make a temporary connection.
bulb	The glass part of an electric lamp, which gives out light when electricity passes through it.
switch	A small control that you use to turn a device on or off.
wire	A long thin piece of metal used to carry an electric current.
buzzer	An electrical device that is used to make a buzzing sound.
motor	A device that uses electricity or fuel to produce movement.